

2/1/19

UNIT - I

* Gate: logic circuit w multiple 'ip' but one o/p


* Basic gates:

1) AND

A	B	Y	
0	0	0	A
0	1	0	B
1	0	0	
1	1	1	

$Y = AB = A \cdot B$

2) OR

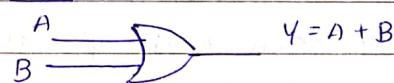

3) NOT

Once complement of given value

$$A \rightarrow Y = \bar{A} \text{ or } A'$$

* Boolean Laws

Commutative

1) $A + B = B + A$

Associative

2) $A + (B+C) = (A+B) + C$

Distributive

3) $A(B+C) = AB + AC$

4) $A + 0 = A$

5) $A + 1 = 1$

6) $A + A = A$

7) $A + \bar{A} = 1$

Duality Theorem

$AB = BA$

$A(BC) = (AB)C$

$A+BC = (A+B)(A+C)$

$A \cdot 1 = A$

$A \cdot 0 = 0$

$A \cdot A = A$

$A \cdot \bar{A} = 0$

$$8) \bar{\bar{A}} = A$$

$$9) (\bar{A} + \bar{B}) = \bar{A} \cdot \bar{B}$$

$$\bar{A}\bar{B} = \bar{A} + \bar{B}$$

$$10) A + AB = A$$

$$A(A + B) = A$$

$$11) A + \bar{A}B = A + B$$

$$A(\bar{A} + B) = AB$$

$$12) AB + A\bar{B} = A$$

$$(A + B)(A + \bar{B}) = A$$

* Duality Theorem

States that starting w a boolean relation

another boolean relationship can be

obtained by 1) changing each OR operator
to an AND OPERATOR

2) changing each AND op. to OR op.

3) Complementing any 0 or 1 in the
expression

Q Simplify the following boolean functions
by applying boolean laws

$$\rightarrow A(\bar{A} + C)(\bar{A}B + C)(\bar{A}BC + \bar{C}) = 0$$

$$\rightarrow (A\bar{A} + AC)(\bar{A}B\bar{A}BC + \bar{A}B\bar{C})(\bar{A}BC + C\bar{C})$$

$$(0 + AC)(\bar{A}BC + \bar{A}B\bar{C})(\bar{A}BC + 0)$$

$$(AC\bar{A}BC + AC\bar{A}B\bar{C})(\bar{A}BC)$$

$$(0 + 0)(\bar{A}BC)$$

$$0(\bar{A}BC)$$

0

In exam write the how that is used

$$2) A\bar{B} + AB + BC$$

$$A(\bar{B} + B) + BC$$

$$A + BC$$

$$3) \bar{A}BC + A\bar{B}C + ABC\bar{C} + ABC$$

$$C(\bar{A}B + A\bar{B}) + AB$$

EXOR

$$\bar{A}BC + ABC + A\bar{B}C + ABC + AB\bar{C} + ABC$$

$$BC(\bar{A} + A) + AC(\bar{B} + B) + AB(\bar{C} + C)$$

$$BC + AC + AB$$

$$4) ABC + \bar{A}\bar{B} + B\bar{C}$$

$$B(Ac + \bar{A}\bar{C} + \bar{C})$$

$$5) (\overline{A+B})(\overline{\bar{A}+\bar{B}})$$

$$\bar{A} \cdot \bar{B} (\bar{\bar{A}\bar{B}})$$

$$\bar{A} \cdot \bar{B} (AB)$$

0

$$6) \overline{\bar{A}\bar{B}} + \overline{\bar{A}B} = (\bar{A} + \bar{B})(\bar{\bar{A}} + \bar{B})$$

$$\bar{A}B + A\bar{B} = (\bar{A} + B)(A + \bar{B})$$

$$A \cdot A + \bar{A}\bar{B} + BA + \bar{B}B$$

$$\bar{A}\bar{B} + AB$$


Q Prove that

$$\begin{aligned} 1) \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} &= \bar{A} \\ \rightarrow \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \\ &\quad \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} \\ \Rightarrow \bar{A}\bar{B}\bar{C} + \bar{A}\bar{C}(B+\bar{B}) + \bar{A}(BC+\bar{B}\bar{C}) \\ &\quad + \bar{B}\bar{C}(A+\bar{A}) \\ &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{C} + \bar{A} + \bar{B}\bar{C} \\ &= \bar{A}(BC + \bar{C} + 1) + (\bar{B}\bar{C}) \\ &= \bar{A} \quad \text{LC(B)} \end{aligned}$$


* Universal Gates

NAND, NOR


1) NAND as AND

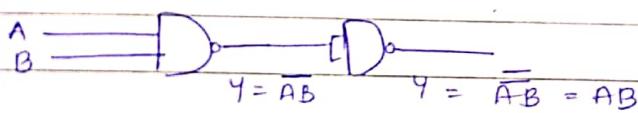

2) NAND as OR

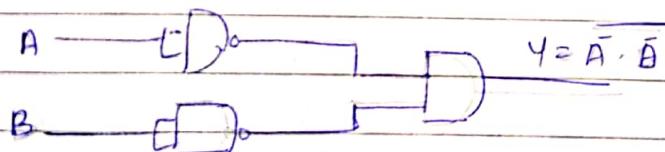


3) NAND as NOT

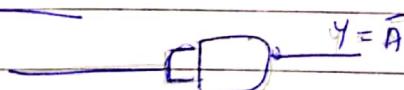


① NOR as AND

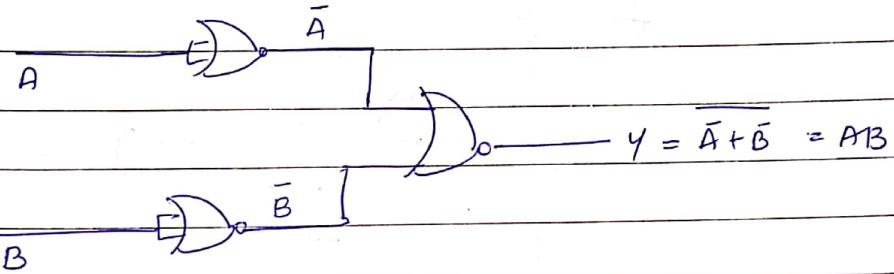
$$\overline{A + B} = \bar{\bar{A}} \cdot \bar{\bar{B}} = AB$$



② NOR as OR

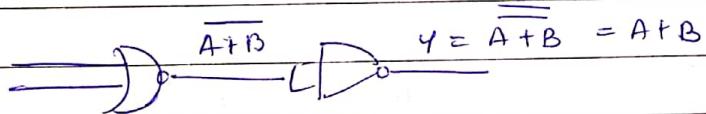


③ NOR as NOT

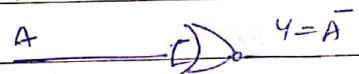

Q) Realize the given boolean expressions using basic gates.

D) $Y = AB + C$


A B C

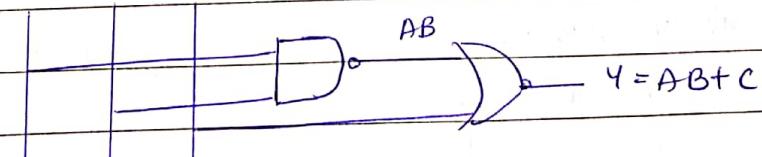

$$2) F = \bar{A}B + A\bar{B}$$

$$F = \bar{A}\bar{B} + A\bar{B}$$

A B C

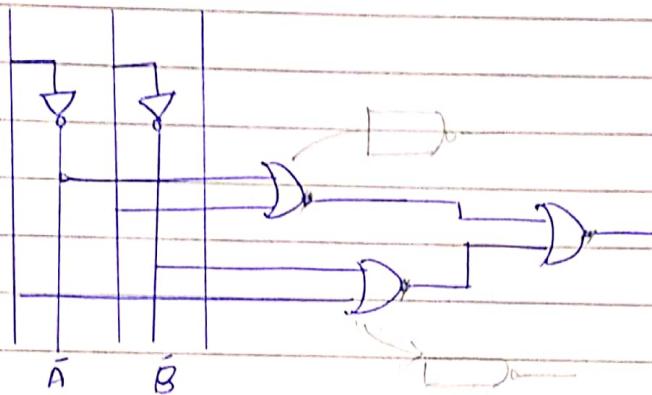

$$3) Z = ABC\bar{C} + AB\bar{C}C + ABC$$


$$ABC + ABC\bar{C} + ABC + A\bar{B}\bar{C} + ABC$$

$$AB(C + \bar{C}) + AC(B + \bar{B}) + ABC$$

$$AB + AC + ABC$$


$$A(B + C + BC)$$


A B C

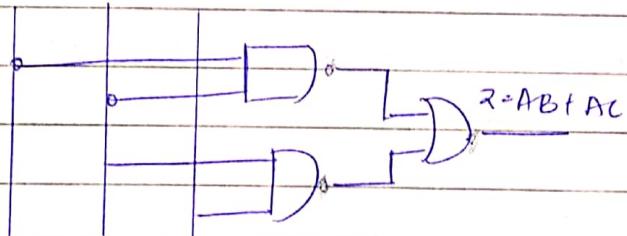


$$4) Y = AB + C \text{ (using NAND gates only)}$$

A B C

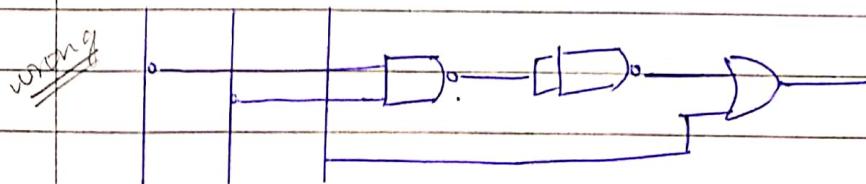

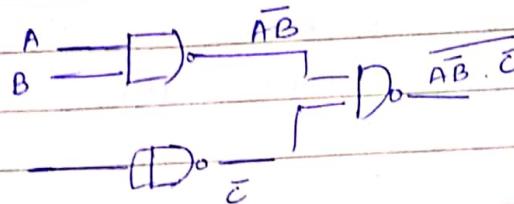

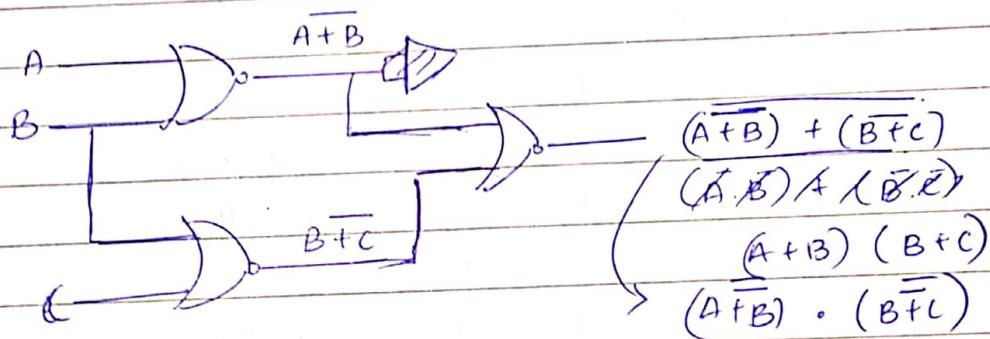a) Realize the given expression $(A+B)(B+C)$ using NOR gate



* Sum of Product (SOP)

A	B	C	Y	
0	0	0	0	
0	0	1	1	$\bar{A}\bar{B}C$
0	1	0	1	$\bar{A}B\bar{C}$
0	1	1	1	$\bar{A}BC$
1	0	0	1	$A\bar{B}\bar{C}$
1	0	1	1	$A\bar{B}C$
1	1	0	1	ABC
1	1	1	1	

minterms

$$Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + ABC + A\bar{B}C$$

$$= \sum m (1, 2, 3, 4, 5, 6, 7)$$

$$= \sum [m_1 + m_2 + m_3 + m_4 + m_5 + m_6 + m_7]$$

Product term: The combination of all variables

Min term: " where the product gives high o/p.

Q Write the expression for the o/p Y given in the truth table

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

$$\rightarrow Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}C$$

$$= \sum m (1, 3, 5)$$

Q Write down all the product terms for two variable boolean function

$$\rightarrow A \ B \ Y$$

0	0	X	$\bar{A}\bar{B} m_0$	product terms
0	1	X	$\bar{A}B m_1$	
1	0	X	$A\bar{B} m_2$	
1	1	X	$AB m_3$	

9

Convert the given expression in standard SOP

$$1. AC + AB + BC$$

$$\rightarrow AC(B + \bar{B}) + AB(C + \bar{C}) + BC(A + \bar{A})$$

$$ACB + AC\bar{B} + ABC + A\bar{B}C + ABC + A\bar{B}\bar{C}$$

$$ABC + AC\bar{B} + A\bar{B}C + A\bar{B}\bar{C}$$

$$2. F(A, B, C) = \bar{A}B + BC$$

$$\rightarrow = \bar{A}B(C + \bar{C}) + BC(A + \bar{A})$$

$$= \bar{A}BC + \bar{A}B\bar{C} + BCA + BCA$$

$$= \bar{A}BC + \bar{A}B\bar{C} + BCA$$

Q* K-Map Reduction Technique

2 variable

	A	B	0	1
0			$\bar{A}\bar{B}$	$\bar{A}B$
1			$A\bar{B}$	AB

m_0 m_1

m_2 m_3

3 variable

A	BC	00	01	11	10
D		$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}I$	$\bar{A}I\bar{C}$	$\bar{A}B\bar{I}$
		m ₀	m ₁	m ₃	m ₂

1		$A\bar{B}\bar{C}$	$A\bar{B}I$	$AB\bar{C}$	$AB\bar{I}$
		m ₄	m ₅	m ₇	m ₆

4 variable

AB	CD	00	01	11	10
		$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}D$	$\bar{A}\bar{B}CD$	$\bar{A}\bar{B}C\bar{D}$
00		m ₀	m ₁	m ₃	m ₂

01		$\bar{A}\bar{B}\bar{C}D$	$\bar{A}\bar{B}CD$	$\bar{ABC}D$	$\bar{ABC}\bar{D}$
		m ₄	m ₅	m ₇	m ₆

11		$ABC\bar{D}$	$AB\bar{C}D$	$ABCD$	$ABC\bar{D}$
		m ₁₁	m ₁₃	m ₁₅	m ₁₄

10		$\bar{ABC}D$	$\bar{ABC}\bar{D}$	$A\bar{B}CD$	$A\bar{B}C\bar{D}$
		m ₈	m ₉	m ₁₁	m ₁₀

q) Plot the value in the K Map for the truth given below

A	B	Y	A	B	0	1
0	0	0				
0	1	1	0	0	0	1
1	0	1				
1	1	0	1	1	1	0

— / — / —

2) A B C Y

0 0 0 0

0 0 1 1

0 1 0 0

0 1 1 0

1 0 0 1

1 0 1 0

1 1 0 0

1 1 1 1

A BC 00 01 11 10

0	0	1	0	0
	m0	m1	m3	m2

1	1	0	0	1
	m4	m5	m7	m6

3) A B C D Y

0 0 0 0 0 11 00 1

0 0 0 1 1 1 11 01 0

0 0 1 0 0 0 11 10 0

0 0 1 1 0 0 0 11 11 1

0 1 0 0 0 0

0 0 0 1 1

0 1 1 0 1

0 1 1 1 0

1 0 0 0 1

1 0 0 1 1

1 0 1 0 0

1 0 1 1 0

		CD	00	01	11	10
		AB	00	01	11	10
00	01	00	0 _{m0}	1 _{m1}	0 _{m2}	0 _{m3}
		01	0 _{m4}	1 _{m5}	0 _{m6}	1 _{m7}
11	10	11	1 _{m8}	0 _{m9}	1 _{m10}	0 _{m11}
		10	1 _{m8}	1 _{m9}	0 _{m10}	0 _{m11}

Q Represent the given std. SOP function on KMap.

$$F(A, B, C) = \bar{A}BC + ABC\bar{C} + ABC \\ = \Sigma m(3, 6, 7)$$

		BC	00	001	11	10	
		A	0	0 _{m0}	0 _{m1}	1 _{m3}	0 _{m2}
0	1	0	m ₄	0 _{m5}	1 _{m7}	1 _{m6}	
		1	m ₀	m ₁	m ₃	m ₂	

Q Plot the Kmap for the given boolean function

$$F(A, B, C) = \bar{A}B(C + \bar{C}) + AC(B + \bar{B}) \\ = \bar{A}BC + \bar{A}B\bar{C} + ACB + A\bar{C}\bar{B} \\ = \Sigma m(3, 2, 7, 5)$$

		BC	00	01	11	10	
		A	0	0 _{m0}	0 _{m1}	1 _{m3}	1 _{m2}
0	1	0	0 _{m4}	1 _{m5}	1 _{m7}	0 _{m6}	
		1	m ₀	m ₁	m ₃	m ₂	

* Grouping Cells for Simplification

D) Grouping two adjacent one (pair) (eliminates one variable)

(i) Horizontally adjacent ones

		BC		00	01	11	10	
		A		0	0	1	1	0
			1	0	0	0	0	
<i>Take common</i>	0							
	1							

$$Y = \bar{A}C$$

(ii) Vertically

		BC		00	01	11	10	
		A		0	0	1	0	0
			1	0	1	0	0	
	0							
	1							

$$Y = \bar{B}C$$

		BC		00	01	11	10	
		A		0	0	0	0	
			1	0	0	1		
	0							
	1							

$$Y = A\bar{C}$$

		CD		00	01	11	10	
		AB		0	(1)	0	0	
			0	0	0	0	0	
(iv)	00							
	01							
	11							
	10							

$$Y = \bar{B}\bar{C}\bar{D}$$

2) Two overlapping pairs

	A	BC	00	01	11	10
①	0		0	1	1	0
	0	0	0	1	1	0
	1	0	0	1	1	0

$$Y = \bar{A}C + BC$$

	A	BC	00	01	11	10
②	0		0	1	1	0
	1	0	0	1	1	0

$$Y = \bar{A}C + AB$$

	A	BC	00	01	11	10
③	0		0	0	0	1
	1	1	0	0	0	1

$$Y = B\bar{C} + A\bar{C}$$

3) Group of four ones (Quad) : eliminans
two variables

	A	B	0	1
0	0		1	1
1	1	1	1	1

$$Y = I$$

	A	BC	00	01	11	10
0	0		0	0	0	0
1	1	1	1	1	1	1

$$Y = A$$

	AB	CD	00	01	11	10
00					1	
01				1	1	
11					1	
10					1	

$$Y = CD$$

"my horizontal"

	AB 00	01	11	10
CD 00	1	0	0	1
1	1	0	0	1

$$Y = \bar{C}$$

(ii) corners for quad

$$Y = \bar{B}\bar{D}$$

1	1	1
1	1	1

+ in centre

$$Y = \bar{B}\bar{D} + BD$$

1	1	1
1	1	1
1	1	1
1	1	1

3) Group of eight ones (octet) : eliminates three variables.

$$\textcircled{1} Y = D$$

1	1	1
1	1	1
1	1	1
1	1	1
1	1	1

$$\textcircled{2} Y = \bar{B}$$

$$\textcircled{3} Y = B$$

$$\textcircled{4} Y = \bar{D}$$

$$\textcircled{2} Y = \bar{B}$$

1	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

$$\textcircled{4} Y = \bar{D}$$

1	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

$$\textcircled{3}$$

1	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

$$Y = B$$

Q Simplify the given boolean expression using K-map reduction technique.

000 m₀

$$1. Y = A\bar{B}C + \bar{A}\bar{B}C + \bar{A}BC + AB\bar{C} + \bar{A}\bar{B}\bar{C}$$

001 m₁

$$101 + 001 + 011 + 100 + 000$$

010 m₂

$$\Sigma m(5, 1, 3, 4, 0)$$

011 m₃

100 m₄

	A \ BC	00	01	11	10
0	1	1	1	0	
1	0	1	3	2	
	4	5	1	6	

$$Y = A\bar{B} + \bar{A}C$$

$$2. Y = Y(A, B, C) = \bar{A}B + \bar{B}C + AB$$

$$\rightarrow \bar{A}B(C + \bar{C}) + (A + \bar{A})\bar{B}C + AB(C + \bar{C})$$

$$\rightarrow \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C + \bar{A}\bar{B}C +$$

$$ABC + AB\bar{C}$$

$$\rightarrow 011 + 010 + 101 + 001 +$$

$$111 + 110$$

$$\rightarrow \Sigma m(3, 2, 5, 1, 7, 6)$$

	A \ BC	00	01	11	10
0	0	1	1	1	1
1	+	1	5	1	6

$$Y = C + B$$

— / —

Q Plot K-map for the given truth table & obtain the reduced K-map boolean expression

① A B C Y

0 0 0 1 m₀

0 0 1 0 m₁

0 1 0 0 m₂

0 1 1 1 m₃

1 0 0 1 m₄

1 0 1 0 m₅

1 1 0 0 m₆

1 1 1 1 m₇

A \ BC	00	01	11	10
0	1 ₀	0 ₁	1 ₂	0 ₂
1	1 ₄	0 ₅	1 ₇	0 ₆

$$Y = \bar{B}\bar{C} + BC$$

② $Y = \bar{A}\bar{B}\bar{C}D + AB\bar{C}\bar{D} + A\bar{B}C\bar{D} + A\bar{B}CD + A\bar{B}\bar{C}\bar{D} +$
 $AB\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}\bar{D}$

$$\rightarrow 0011 + 1110 + \cancel{0101} + 1010 + 1000 +$$

$$1100 + 0011 + 0000$$

$$\rightarrow \Sigma m(2, 14, 10, 11, 8, 12, 3, 0)$$

AB \ CD	00	01	11	10
00	1 ₀	2	1 ₃	1 ₂
01	4	5	7	6
11	1 ₁₂	1 ₁₃	1 ₁₅	1 ₁₄
10	1 ₈	9	1 ₁₁	1 ₁₀

$$Y = \bar{B}\bar{D} + \bar{B}CD + ABD +$$

$$+ AD + \bar{BC}$$

$$3) Y = \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + A\bar{B}C\bar{D} + A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D$$

5>

$\Sigma m (2, 4, 5, 9, 12, 13)$

		CD		AB			
		00	01	11	10		
00	0	0 ₂	3	1 ₂			
	1 ₄	1 ₅	7	6			
01	1 ₁₂	1 ₁₃	15	14			
	8	1 ₉	11	10			

$$Y = B\bar{C} + A\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D}$$

$$\begin{aligned} 2) F &= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}D + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + \\ &\quad \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + AB\bar{C}\bar{D} + \\ &= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}D + AB\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + \\ &\quad AB\bar{C}\bar{D} \\ &= \Sigma m (1, 5, 8, 2, 10, 6) \end{aligned}$$

		CD		AB			
		00	01	11	10		
00	0	1 ₁	3	1 ₂			
	4	1 ₅	7	1 ₆			
01	12	13	15	14			
	1 ₆	9	11	1 ₁₀			

$$Y = \bar{A}\bar{C}D + \bar{A}C\bar{D} + \bar{A}\bar{B}\bar{D}$$

$$5) \quad \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC$$

$$001 + 000 + 100 + 101 + 011$$

$$m_1 + m_0 + m_4 + m_5 + m_3$$

		$\bar{B}C$	00	01	11	10
000	0	1	0	1	1	2
001	1	1	0	1	0	1
010	0	1	0	1	1	2
011	1	1	0	1	0	1
100	1	1	0	1	1	2
101	0	1	0	1	1	2
110	1	1	0	1	1	2
111	0	1	0	1	1	2

$$y = \bar{B} + \bar{A}C$$

$$6) \quad Y = \bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + A\bar{B}CD +$$

$$+ \bar{A}\bar{B}\bar{C}\bar{D} + ABC\bar{D} + \bar{A}BC\bar{D} + A\bar{B}C\bar{D}$$

$$= A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + A\bar{B}CD$$

$$+ \bar{A}\bar{B}\bar{C}\bar{D} + ABC\bar{D} + \bar{A}BC\bar{D} + A\bar{B}C\bar{D}$$

$$= 0111000 + 0000 + 0100 + 1100 + 0011 + 1011$$

$$+ 0010 + 1110 + 0110 + 1010$$

$$= \Sigma m(8, 0, 4, 12, 3, 11, 2, 14, 6, 10)$$

AB	CD	00	01	11	10			
00	0	1	0	2	1	3	1	2
01	1	4	5	7	1	6		
11	1	1	2	3	5	1	14	
10	1	3	9	11	1	10		

$$Y = \bar{D} + \bar{C}\bar{E}$$

1/1

⇒ Don't care condition

- Q Plot the k-map for the given truth table & obtain the reduced boolean expression

A B C Y

0 0 0 0

0 0 1 1

0 1 0 0

0 1 1 1

1 0 0 0

1 0 1 1

1 1 0 X

1 1 1 X

		BC		AB	
		00	01	11	10
A	B	0	1	1	0
		1	1	X	X
		Y = C			

- Q Find the reduced SOP for the given boolean expression

$$F(A, B, C, D) = \sum m(1, 3, 7, 12, 15) + \sum d(0, 2, 4)$$

		CD		AB	
		00	01	11	10
A	B	00	X	1	1
		01	X	1	
A	B	11		1	
		10		1	

$$Y = \bar{A}\bar{B} + \bar{C}D$$

$$0-5 \Rightarrow 0 \quad 6-9 \Rightarrow 1$$

Q The input to a combinational logic circuit is a valid single digit BCD data. Design the logic circuit using minimum hardware to detect whenever a number greater than 5 appears at the input.

	A	B	C	D	Y
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	X
11	1	0	1	1	X
12	1	1	0	0	X
13	1	1	0	1	X
14	1	1	1	0	X
15	1	1	1	1	X

— / —

⇒ Product of Sum

	<u>Minterms</u>	A B C	<u>Minterms</u>
M_0	$A + B + C$	0 0 0	$\bar{A} \bar{B} \bar{C}$
M_1	$A + B + \bar{C}$	0 0 1	$\bar{A} \bar{B} C$
M_2	$A + \bar{B} + C$	0 1 0	$\bar{A} B \bar{C}$
M_3	$A + \bar{B} + \bar{C}$	0 1 1	$\bar{A} B C$
M_4	$\bar{A} + B + C$	1 0 0	$A \bar{B} \bar{C}$
M_5	$\bar{A} + B + \bar{C}$	1 0 1	$A \bar{B} C$
M_6	$\bar{A} + \bar{B} + C$	1 1 0	$A B \bar{C}$
M_7	$\bar{A} + \bar{B} + \bar{C}$	1 1 1	$A B C$

Q. $Y = \pi M (0, 1, 2, 3, 4, 5, 7)$

AB		CD	00	01	11	10
0	1	00	0	0	0	0
1	0	01	0	0	0	1

$Y = A \times (B) \times \bar{C}$

Step 1

Q. $Y = \pi M (0, 1, 2, 4, 5) + \pi d (8, 9, 11, 12, 13, 15)$

AB		CD		00	01	11	10
00	01	00	0	0	3	0	2
01	10	01	0	5	7	6	
11	10	X	X ₁₂	X ₁₃	X ₁₅	X ₁₄	
10	11	X	X ₈	X ₉	X ₁₁	X ₁₀	

$Y = C_d (A + B + D)$

→ Quine McCluskey Reduction Technique

Q. $Y(A, B, C, D) = \sum m(0, 1, 3, 7, 8, 9, 11, 13)$
 $0000, 0001, 0011, 0111, 1000, 1001,$
 $1011, 1111$

Step 0	Group	Minterms	Ymin
	0	0	0 0 0 0 ✓
	1	1	0 0 0 1 ✓
	2	8	1 0 0 0 ✓
	3	3	0 0 1 1 ✓
	4	9	1 0 0 1 ✓✓
	5	7	0 1 1 1 ✓✓
	6	11	1 0 1 1 ✓✓
	7	15	1 1 1 1 ✓✓

Step 1	Group	Minterms	Ymin
	0	(0, 1)	0 0 0 0 ✓
		(0, 8)	- 0 0 0 ✓
	1	(1, 3)	0 0 - 1 ✓
		(1, 9)	- 0 0 1 ✓
		(8, 9)	1 0 0 - ✓
	2	(3, 7)	0 - 1 1 ✓
		(3, 11)	- 0 1 1 ✓
		(9, 11)	1 0 - 1 ✓
	3	(7, 15)	- 1 1 1 ✓
		(11, 13)	1 - 1 1 ✓

1 / 1

\Rightarrow Karnaugh Minimization Technique

Minterms

m_0
 m_1
 m_2
 m_3
 m_4
 m_5
 m_6
 m_7
 m_8
 m_9
 m_{10}
 m_{11}
 m_{12}
 m_{13}
 m_{14}
 m_{15}

q. $Y(A, B, C, D) = \Sigma m(0, 1, 3, 7, 8, 9, 11, 15)$

0000, 0001, 0011, 0111, 1000, 1001,
1011, 1111

Step 0

Group	Minterms	Variables
0	0	A B C D 0 0 0 0 ✓
1	1	0 0 0 1 ✓
	8	1 0 0 0 ✓
2	3	0 0 1 1 ✓
	4	1 0 0 1 ✓
3	7	0 1 1 1 ✓
	11	1 0 1 1 ✓
4	15	1 1 1 1 ✓

Step 1

Group	Minterms	Variables
0	(0, 1)	A B C D 0 0 0 - ✓
	(0, 8)	- 0 0 0 ✓
1	(1, 3)	0 0 - 1 ✓
	(1, 9)	- 0 0 1 ✓
	(8, 9)	1 0 0 - ✓
2	(3, 7)	0 - 1 1 ✓
	(3, 11)	- 0 1 1 ✓
	(9, 11)	1 0 - 1 ✓
3	(7, 15)	- 1 1 1 ✓
	(11, 15)	1 - 1 1 ✓

Step 2

Group	Minterms	Variables	Group
0	(0, 1, 8, 9)	- 0 0 -	$\bar{B} \bar{C}$
	(0, 8, 1, 9)	- 0 0 -	
1	(1, 3, 9, 11)	- 0 - 1	$\bar{B} D$
	(1, 9, 3, 11)	- 0 - 1	
2	(3, 7, 11, 15)	- - 1 1	$C D$
	(3, 11, 7, 15)	- - 1 1	

Prime Implicants Chart

PI terms	Groups	Minterms							
		0	1	3	7	8	9	11	15
$\bar{B} \bar{C}$	$\leftarrow 0, 1, 8, 9 \leftarrow$	(X)	X			(X)	X		
$\bar{B} D$	$1, 3, 9, 11$		X	X			X	X	
$C D$	$\leftarrow 3, 7, 11, 15 \leftarrow$			X	(X)		X		(X)

$$Y = \bar{B} \bar{C} + C D \text{ are essential prime implicants}$$

Q Minimize the given boolean exp

$$F(A, B, C, \bar{D}) = \Sigma m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$$

0000, 0001, 0010, 0011, 0101, 0111, 1000, 1001,
1011, 1101 1110

STEP 0

Group	Minterm	Variables
0	0	A B C P 0 0 0 0 ✓
1	1	0 0 0 1 ✓
2		0 0 1 0 ↙
8	1000	1 0 0 0 ✓

— / —

Group	Minterm	Variables	
2	3	A B C D 0 0 1 1	✓
	5	0 1 0 1	✓
	9	1 0 0 1	✓
3	7	0 1 1 1	✓
	11	1 0 1 1	✓
	14	1 1 1 0	,

STEP 1

Group	Minterms	Variables	
0	(0, 1)	A B C D 0 0 0 -	
	(0, 2)	0 0 - 0	
	(0, 3)	- 0 0 0	
1	(1, 3)	0 0 - 1	
	(1, 5)	0 - 0 1	
	(1, 9)	- 0 0 1	
2	(2, 3)	0 0 1 -	
	(8, 9)	1 0 0 -	
	(3, 7)	0 - 1 1	
3	(3, 11)	- 0 1 1	
	(5, 7)	0 1 - 1	
	(9, 11)	1 0 - 1	

1 / 1

STEP 2	Group	Minterms
0	0, 1, 2, 3	
	0, 2, 1, 3	
	0, 1, 8, 9	
	0, 8, 1, 9	
1	1, 3, 5, 7	
	1, 5, 3, 7	
	1, 9, 3, 11	
	1, 3, 9, 11	

Variables

$$\begin{array}{cccc} A & B & C & D \\ 0 & 0 & - & - \end{array} \quad] \bar{A}\bar{B}$$

$$00 - -$$

$$\begin{array}{ccc} - & 00 & - \\ - & 00 & - \end{array} \quad] \bar{B}\bar{C}$$

$$-00-$$

$$\begin{array}{cc} 0 & -1 \\ 0 & -1 \end{array} \quad] \bar{A}D$$

$$0 - - 1$$

$$\begin{array}{cc} - & 0 - 1 \\ - & 0 - 1 \end{array} \quad] \bar{B}D$$

$$-0 - 1$$

$$Q. Y(A, B, C, D) = E$$

STEP 0 Group

0

2

3

4

Prime Implicant's Chart

PI terms	Groups	Minterms							
		0	1	2	3	5	7	8	9
$\bar{A}\bar{B}$	0, 1, 2, 3	x	x	(x)	x				
$\bar{B}\bar{C}$	0, 1, 8, 9	x	x					(x)	
$\bar{A}D$	1, 3, 5, 7	x			x	(x)	(x)		
$\bar{B}D$	1, 3, 9, 11	x		x					
$A\bar{B}C\bar{D}$									

STEP 1 Group

0

1

2

3

$\Sigma m(1, 3, 7, 11, 15) + \Sigma d(0, 2, 5)$			
Step	Group	Minterms	Variables
0	0*	0000	A B C D
1	1	0001	
	2*	0010	
2	3	0011	
	5*	0101	
3	7	0111	
	11	1011	
4	15	1111	
Step I			
0	0*, 1	000-	A B C D
	0*, 2	00-	
1	1, 3	00-1	
	1, 5*	0-01	
	2*, 3	001-	
2	3, 7	0-11	
	3, 11	-011	
	5*, 7	01-1	
3	7, 15	-111	
	11, 15	1-11	

STEP 2

Group

Minterms

Variables
A B C D

0 0, 1, 2, 3

0 0 --] \bar{AB} 0, 2, 1, 3

0 0 --]

1 1, 3, 5, 7

0 - - 1] \bar{AD} 1, 5, 3, 7

0 - - 1]

2 3, 7, 11, 15

- - 1 1] CD 3, 11, 7, 15

- - 1 1]

STEP 1 Group

1

STEP 2 Group

2

∴ $Y = \bar{AB} + \bar{AD} + CD$

Prime Implicant Chart (Ignore "DON'T CARE")

PI Terms

Groups

Variables
A B C D \bar{AB} \bar{AD}

CD

	0	1	2	3	7	11	15
\bar{AB}	1, 3	x	x				
\bar{AD}	1, 3, 7	x	x	(x)			
CD	3, 7, 11, 15		x	x	(x)	(x)	

because 1, 3, 7 are covered
 $Y = CD + \bar{AD}$ making the exp complete

$$q. Y(A, B, C, D) = \sum m(5, 7, 3, 15)$$

0101, 0111, 0011, 1111

STEP 0 Group

Minterms

A B C D

1 5 0 1 0 1 ✓

3 0 0 1 1 ✓

2 7 0 1 1 1 ✓

4 15 1 1 1 1

	Group	Minterms	A B C D	
] $\bar{A}\bar{B}$	1	5, 7	0 1 - 1	$\bar{A}BD$
] $\bar{A}D$		3, 7	0 - 1 1	$\bar{A}CD$
] CD	2	7, 15	- 1 1 1	BCD


	Group	Minterms	A B C D	
Prime Implicant Chart				
PI terms	Groups		5 7 3 15	
$\bar{A}BD$	5, 7	(X)	X	
$\bar{A}CD$	3, 7		X (X)	
BCD	7, 15		X (X)	

$\bar{A}B + \bar{A}D + BCD = \bar{A}BD + \bar{A}CD + BCD$



UNIT II

Data Processing Circuits


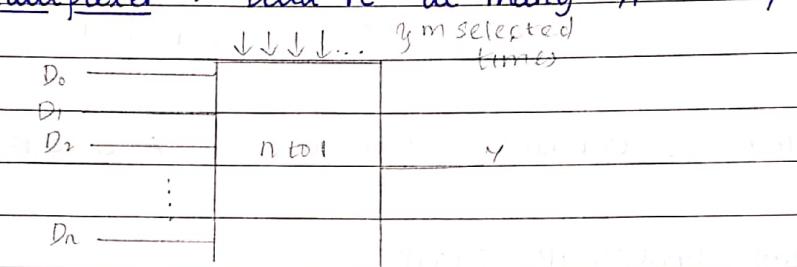
⇒ * Multiplexer : Data Pcs w/ many i/p one o/p




* 2 to 1 multiplexer

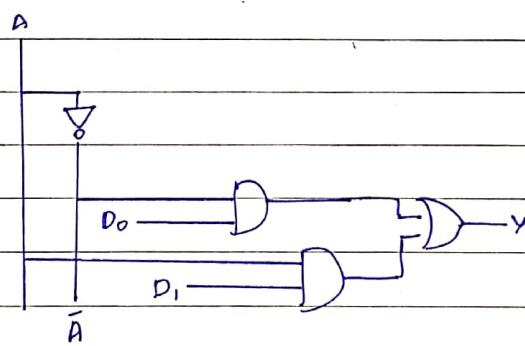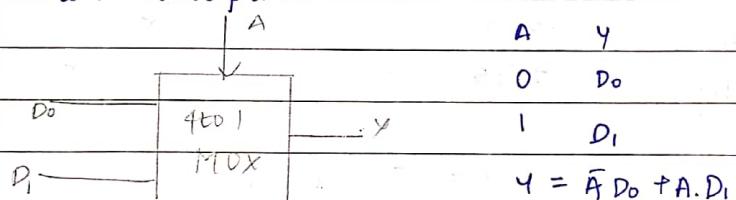


* 4 to 1 MUX

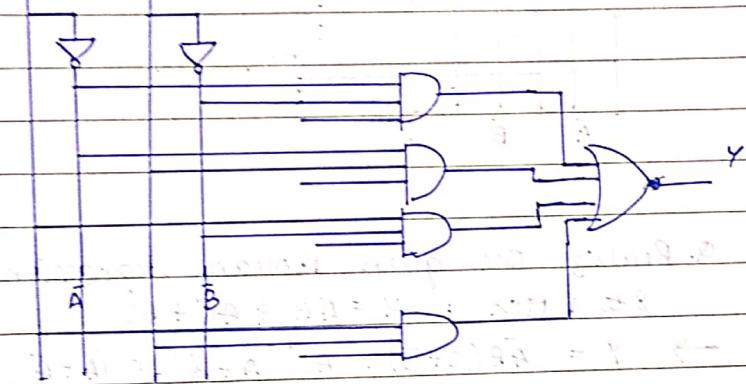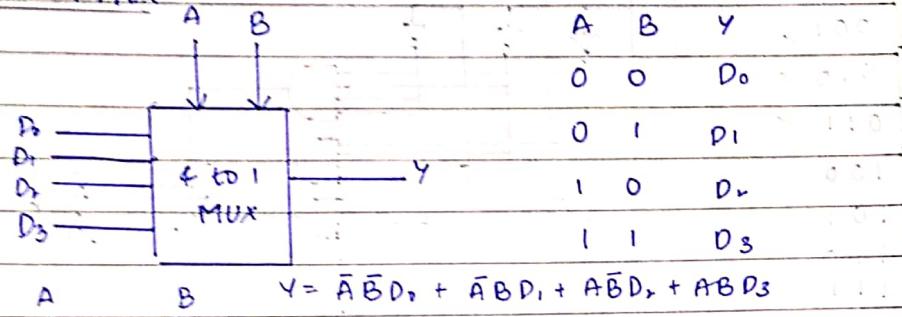

* 8 to 1 MUX

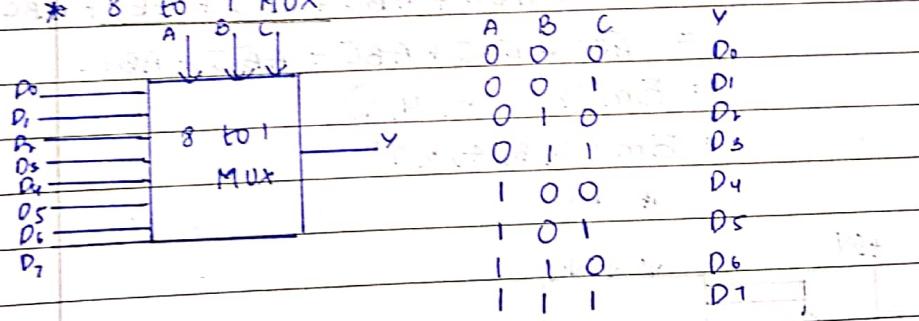

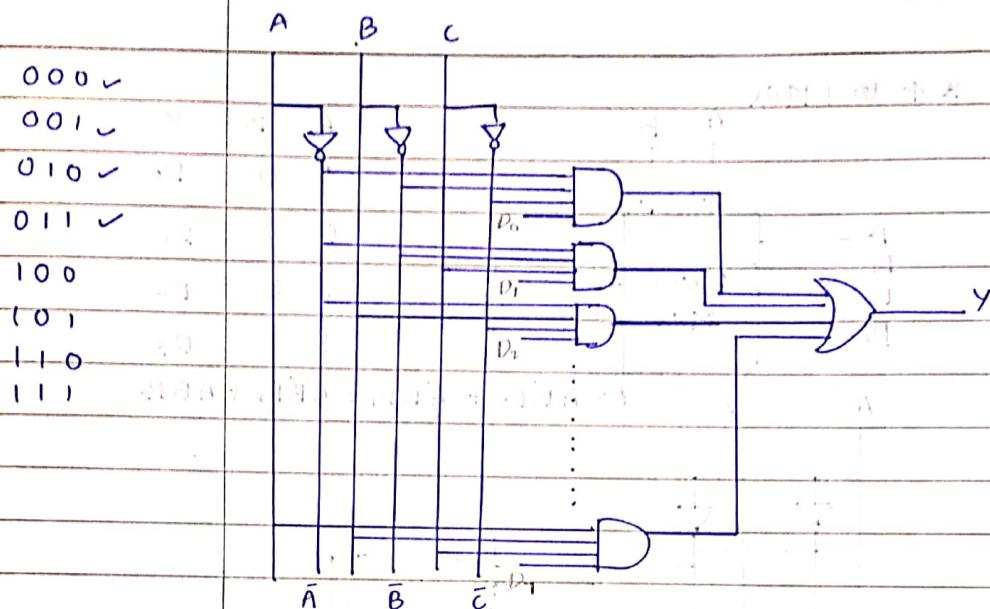
$$Y = \bar{A}\bar{B}\bar{C}D_0 + \bar{A}\bar{B}CD_1 + \bar{A}BC\bar{D}_2 + \bar{A}BCD_3 + A\bar{B}C\bar{D}_4 + A\bar{B}CD_5 + \dots + ABCD_7$$



Q. Realize the given boolean expression using
8 to 1 MUX : $Y = AB + A\bar{C} + BC$
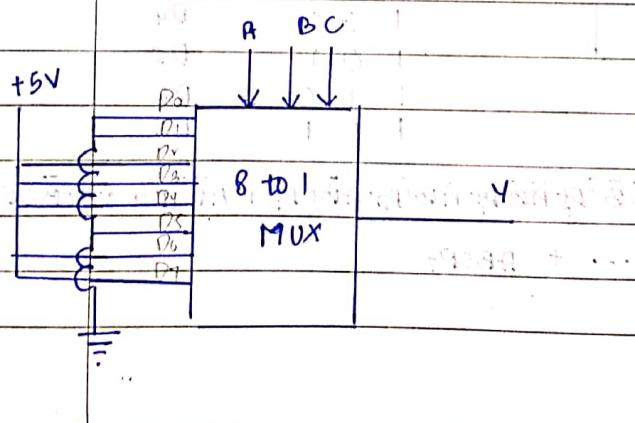
$$\begin{aligned}
 \rightarrow Y &= \bar{A}B(C+\bar{C}) + A\bar{C}(B+\bar{B}) + (A+\bar{A})BC \\
 &= \bar{A}BC + \bar{A}B\bar{C} + ABC + A\bar{B}\bar{C} + ABC + \bar{A}BC \\
 &= \bar{A}BC + \bar{A}B\bar{C} + ABC + A\bar{B}\bar{C} + AB\bar{C} \\
 &= \Sigma m(3, 2, 6, 4, 7) \\
 &= \Sigma m(2, 3, 4, 6, 7)
 \end{aligned}$$





Q) Using 8 to 1 MUX solve $y = \bar{A}B + \bar{B}\bar{C} + ABC$

Realize it using 4 to 1 MUX

$$\begin{aligned} \rightarrow y &= \bar{A}B(C+\bar{C}) + \bar{B}\bar{C}(A+\bar{A}) + ABC \\ &= \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C} + ABC \end{aligned}$$

011 + 010 + 100 + 000 + 111

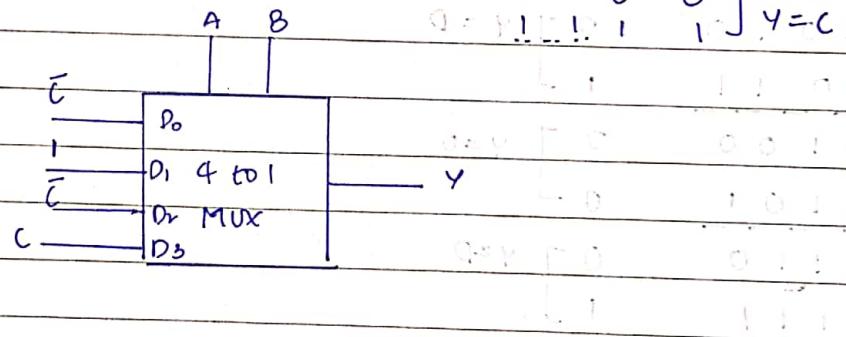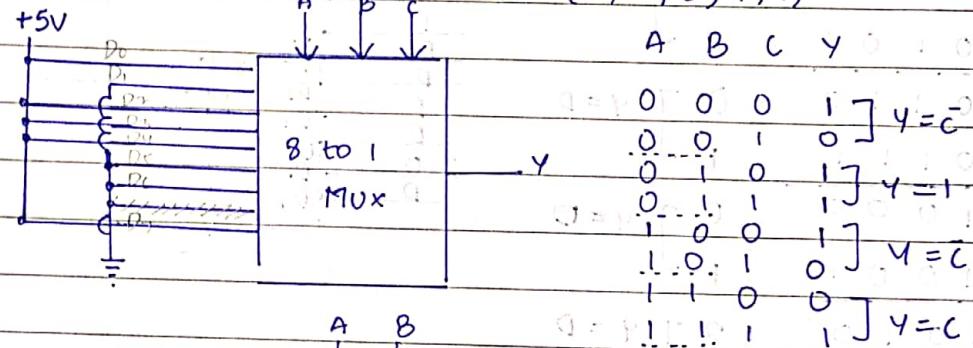
$$E_M(3, 2, u, 0, 7) = E_M(0, 2, 3, 4, 7)$$



Q) Realize the given boolean function


$$Y = (A, B, C, D) = E_M(0, 2, 3, 5, 7, 9, 11, 15)$$

and 8 to 1 MUX.

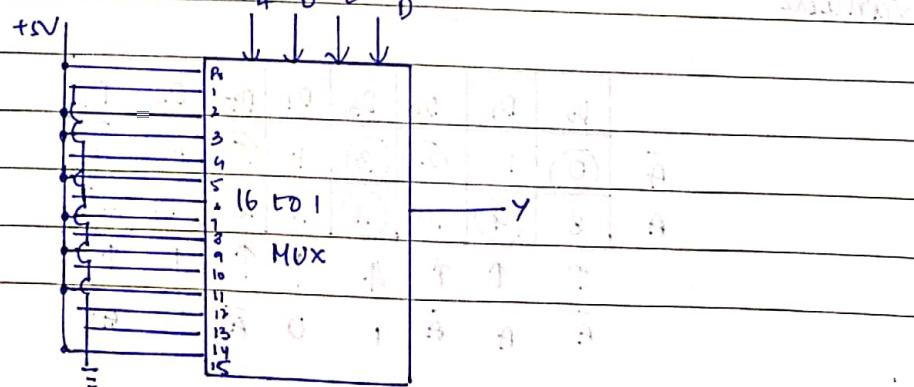

Nikita

A	B	C	D	Y
0	0	0	0	1] $y = D$
0	0	0	1	0] $y = D$
0	0	1	0	1] $y = D$
0	0	1	1	1] $y = D$
0	1	0	0	0] $y = D$
0	1	0	1	1] $y = D$
0	1	1	0	0] $y = D$
0	1	1	1	1] $y = D$
1	0	0	0	0] $y = D$
1	0	0	1	1] $y = D$
1	0	1	0	0] $y = D$
1	0	1	1	1] $y = D$
1	1	0	0	0] $y = D$
1	1	0	1	1] $y = D$
1	1	1	0	0] $y = D$
1	1	1	1	1] $y = D$

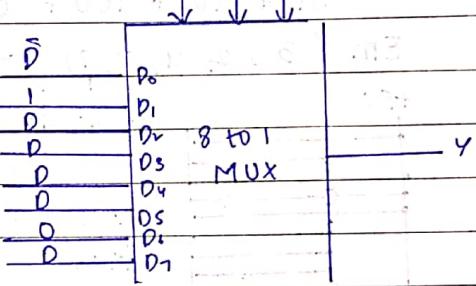

Above same problem, use select line A as mapped entered variable

	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
\bar{A}	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	T	↑	↑	↑	↑	↑	↑	↑
	\bar{A}	A	\bar{A}	1	0	\bar{A}	0	\bar{A}

01 08
Maths
Web
(N) Java

→ implement the
 $F(A, B, C) = \sum m(1, 2, 4)$

Use A as Map

A B C
0 0 0
0 0 1
0 1 0
0 1 1
1 0 0
1 0 1
1 1 0
1 1 1

(ii) A a

Imp

01 08

Maths
Web
(H) Java

(H) Yesterday Web

Java & Web

B C 0
↓ ↓ ↓
A


A		D ₀
A		D ₁
1		D ₂
0	8 to 1	D ₃
0		MUX
1		
1		
1		

Q) Implement the given boolean function using 4:1 MUX

$$F(A, B, C) = \sum m(0, 2, 5, 7). \text{ Use } 'C' \text{ as Map Entered Variable}$$

Use A as Map Entered Variable.

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

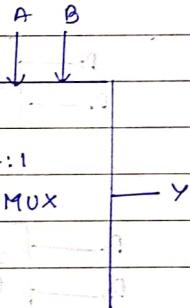

(II) A as MEV

Implementation Table

A	D ₀	D ₁	D ₂	D ₃
0	0	2	3	7

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Q) Realize 4:1 MUX using 2:1 MUX only

2:1 A Y

D₀

D₁

4:1 A B Y

D₀

D₁

D₂

D₃

A B

D₀

D₁

D₂

D₃

4:1

MUX

D₀ 2:1 C

D₁ 2:1 C

D₂ 2:1 C

D₃ 2:1 C

D₄ 2:1 C

D₅ 2:1 C

D₆ 2:1 C

D₇ 2:1 C

B = 0, 1, 0, 1
changes 4 times

D₀

D₁

2:1 MUX

D₀

D₁

Demultiplex

Q) Realize 8:1 MUX using 4:1 MUX's

B ↓ C

D₀ D₁ D₂ D₃ 4:1 MUX Y₀

D₄ D₅ D₆ D₇ 4:1 MUX Y₁

D₈ D₉ D₁₀ D₁₁ 4:1 MUX Y₂

D₁₂ D₁₃ D₁₄ D₁₅ 4:1 MUX Y₃


D₁₆ D₁₇ D₁₈ D₁₉ 4:1 MUX Y₄

D₂₀ D₂₁ D₂₂ D₂₃ 4:1 MUX Y₅



D₂₄ D₂₅ D₂₆ D₂₇ 4:1 MUX Y₆


D₂₈ D₂₉ D₃₀ D₃₁ 4:1 MUX Y₇

1 to 2 MUX

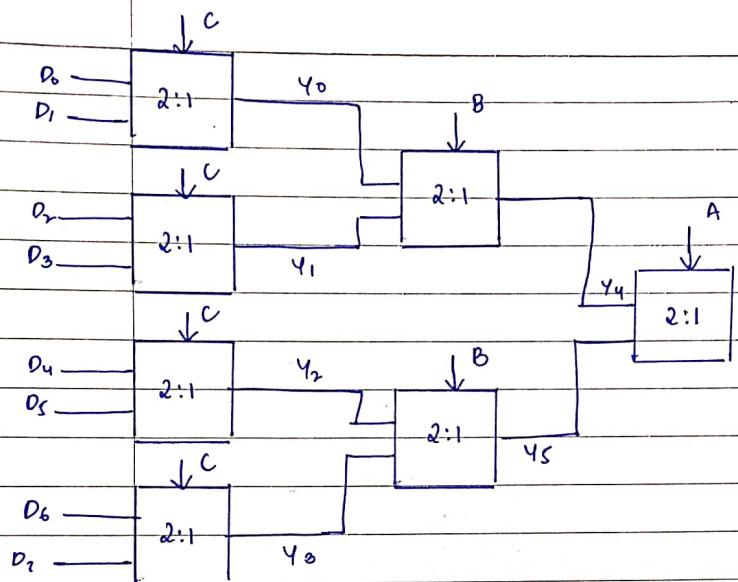

Demultiplexer

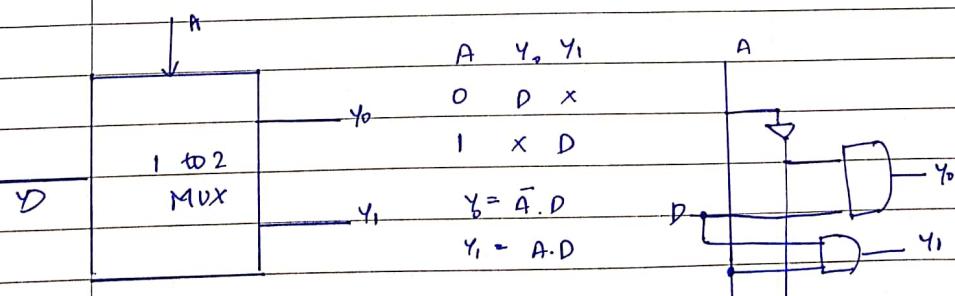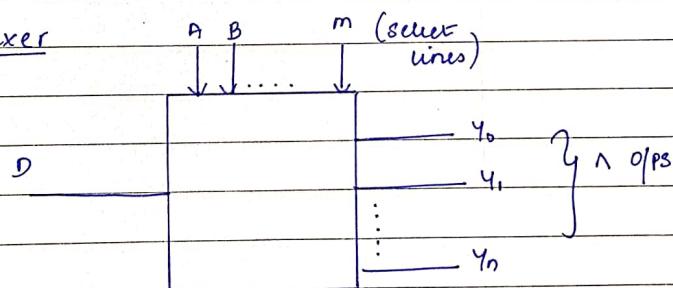


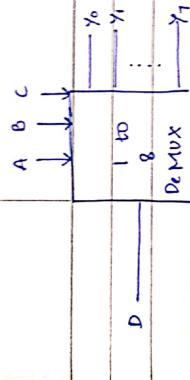

Decorder
A de word
there is
win - 01


Truth Table

A	B	C	Y ₀	Y ₁	Y ₂	Y ₃	Y ₄	Y ₅	Y ₆	Y ₇
0	0	0	D	0	0	0	0	0	0	0
0	0	1	0	D	0	0	0	0	0	0
0	1	0	0	0	D	0	0	0	0	0
0	1	1	0	0	0	D	0	0	0	0
1	0	0	0	0	0	0	D	0	0	0
1	0	1	0	0	0	0	0	D	0	0
1	1	0	0	0	0	0	0	0	D	0
1	1	1	0	0	0	0	0	0	0	D

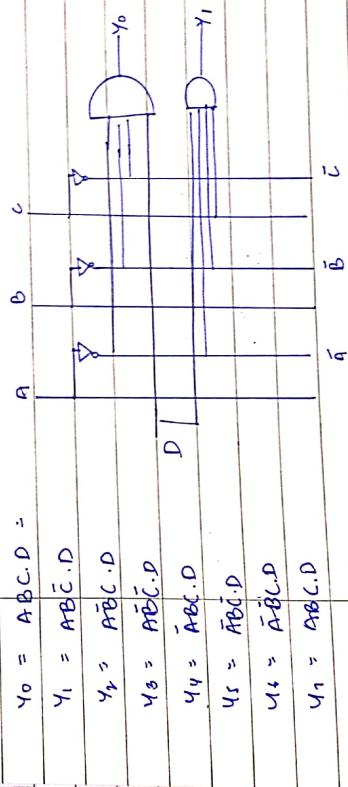

Decoder

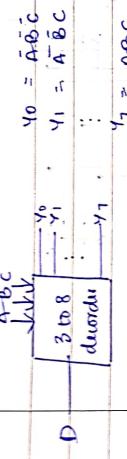A decoder is similar to demux w/o 1 exception that there is no data input. The only i/p are the control lines or select lines.




Similar like last one; only no data line.

Q. Realize the following boolean expression using suitable decoder & multiplex OR GATES.

$$F_1(A, B, C) = \Sigma m(0, 4, 6)$$

$$F_2(A, B, C) = \Sigma m(0, 5)$$

$$F_3(A, B, C) = \Sigma m(1, 2, 3, 7)$$

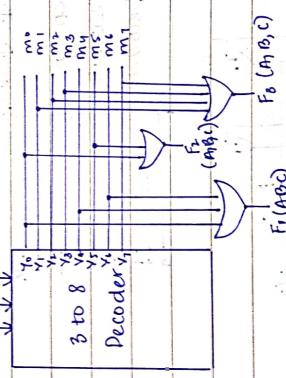

* only OR Gates are used because SOP.

$$q. F_1(A, B) = E_M(0, 1)$$


$$F_2(A \oplus B) = E_M(1, 2)$$

$$F_3(A \oplus B) = E_M(0, 3)$$

Inputs:

A

B

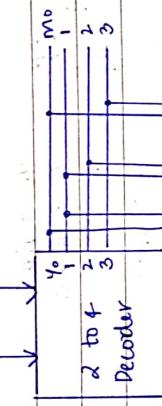

Encoder

n
input

Realize BCD to decimal decoder using suitable decoder

Inputs:

A

B

C

D

Outputs:

Y0

Y1

Y2

Y3

Y4



Y5

Y6


Y7

Y8


Y9

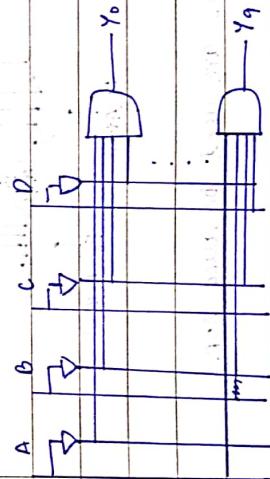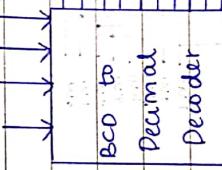

Encoder

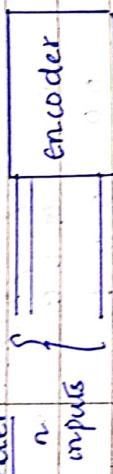


Decimal to m outputs
ex. BCD encoder.

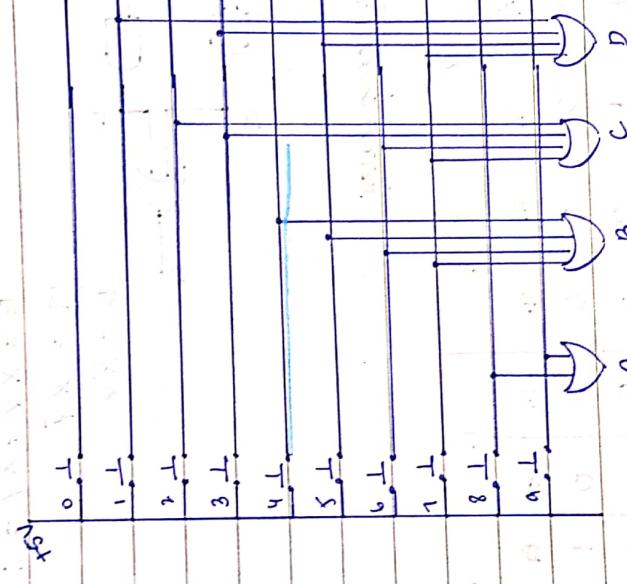

$$\begin{aligned}
 X \oplus Y &= \bar{X}Y + X\bar{Y} \\
 X \odot Y &= \bar{X}\bar{Y} + XY = \overline{\bar{X}Y + X\bar{Y}} = \bar{X}\bar{Y} + XY \\
 X \oplus Y &= \bar{X}Y + X\bar{Y} = \overline{\bar{X}Y + X\bar{Y}} = \bar{X}\bar{Y} + XY \\
 X \odot Y &= (\bar{X}Y)(\bar{X} + \bar{Y}) \\
 &= (\bar{X}Y) \cdot \bar{X}Y \\
 &\Rightarrow (X \oplus Y) \cdot (X \odot Y)
 \end{aligned}$$

Magnitude Comparator

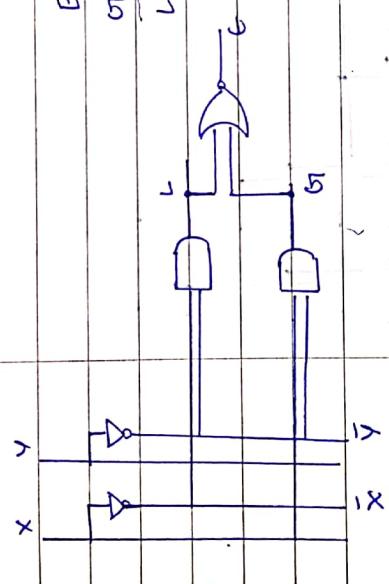

2 bit Magnitude Comparator

X ₁	X ₀	Y ₁	Y ₀	G ₁	L	E	G ₀
0	0	0	0	0	0	1	-
0	0	0	1	0	0	-	0
0	0	1	0	0	1	0	-
0	0	1	1	0	0	0	0
0	1	0	0	1	0	0	-
0	1	0	1	1	0	0	-
0	1	1	0	1	1	0	-
0	1	1	1	1	1	0	-
1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	-
1	0	1	0	0	0	0	-
1	0	1	1	0	0	0	-
1	1	0	0	1	0	0	-
1	1	0	1	1	0	0	-
1	1	1	0	1	1	0	-
1	1	1	1	1	1	0	-

X	χ_0	χ_1	χ_2	χ_3	χ_4	χ_5	χ_6	χ_7	χ_8	χ_9	χ_{10}	χ_{11}	χ_{12}	χ_{13}	χ_{14}	χ_{15}
y	y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7	y_8	y_9	y_{10}	y_{11}	y_{12}	y_{13}	y_{14}	y_{15}
E	E_0	E_1	E_2	E_3	E_4	E_5	E_6	E_7	E_8	E_9	E_{10}	E_{11}	E_{12}	E_{13}	E_{14}	E_{15}

$x_0 \bar{y}_0$	00	01	10	11	y_0	00	01	10	11	$x_0 y_0$	00	01	10	11	$\bar{x}_0 \bar{y}_0$	00	01	10	11
00	0	0	0	0	0	0	0	0	0	00	0	0	0	0	00	0	0	0	0
01	0	0	0	0	0	0	0	0	0	01	0	0	0	0	01	0	0	0	0
10	0	0	0	0	0	0	0	0	0	10	0	0	0	0	10	0	0	0	0
11	0	0	0	0	0	0	0	0	0	11	0	0	0	0	11	0	0	0	0

G_1	$x_1 y_1$							
	0 0	0	0	0	0	0	0	0
	0 0	0	0	0	0	0	0	0
	0 0	0	0	0	0	0	0	0
	0 0	0	0	0	0	0	0	0
G_2	$x_0 y_0 + x_0 y_0$	-	0	0	0	0	0	-
	0 0	0	0	0	0	0	0	0
	0 0	0	0	0	0	0	0	0
	0 0	0	0	0	0	0	0	0
	0 0	0	0	0	0	0	0	0

$$G_1 = \begin{pmatrix} X_1 & X_2 \\ - & - \end{pmatrix}$$

$$x^y \neq$$

17

$$\begin{aligned}
 G_1 &= G_0 + G_1 = X_0 \bar{Y}_0 + X_1 \bar{Y}_1 & A & B \\
 L &= L_0 + L_1 = \bar{X}_0 Y_0 + \bar{X}_1 Y_1 & 0 & 0 \\
 E &= E_0 + E_1 = X_0 X_0 + \bar{X}_0 \bar{Y}_0 + \bar{X}_1 \bar{Y}_1 + X_1 Y_1 & 0 & 0
 \end{aligned}$$

Q3 Design the priority encoder for the truth table given below
Priority of i/p $X_1 > X_2 > X_3$

Inputs			Outputs		
S	X_1	X_2	X_3	A	B
0	x	x	x	0	0
1	1	x	x	0	1
10	0	1	x	1	0
11	0	0	1	1	1
100	0	0	0	0	0
101	0	0	0	0	0
110	0	0	0	0	0
111	0	0	0	0	0

* $f_1 = X_1 X_3$ $f_2 = X_0 X_2$ $f_3 = X_0 X_1$

Q3 Design
A B C

$A = S\bar{X}_1 X_3 + \bar{S}\bar{X}_1 X_2$
 $B = S X_1 + S\bar{X}_2 X_3$
 $C = S\bar{X}_1 (X_3 + X_2)$

1 1 0
1 1 0
0 0 1
0 0 1

— / —

Exclusive OR gate

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

below

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


$$Y = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC$$

$$= \bar{A}(\bar{B}C + BC) + A(\bar{B}C + BC)$$

$$= \bar{A}(B \oplus C) + A(B \oplus C)$$

$$P = A \oplus B \oplus C$$

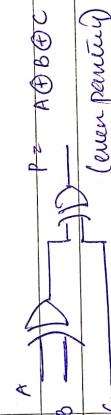- Can be used as parity generator & checker
- Even parity generation



Q2 Design odd parity generator for 3 bit binary data
Input → odd no. of 1
even no. of 0

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + ABC$$

$$= \bar{A}(\bar{B}\bar{C} + BC) + A(\bar{B}\bar{C} + \bar{C}B)$$

$$= \bar{A}(B \oplus C) + A(B \oplus C)$$

$$P = \overline{A \oplus B \oplus C}$$



* Design even parity checker for the data received

$A \ B \ C \ P \ Y_{even}$

* data is not corrupted

$00 \ 000$

* as no. of ones is 0 \rightarrow even but Parity $P=1$

$00 \ 011$

so data is corrupted $\therefore Y=1$ to make it even parity

$00 \ 110$

K-map

$AB \backslash CP$	00	01	11	10
00	0	1	0	1
01	1	0	1	0
11	0	1	0	1
10	1	0	1	0

10100

$$Y = \bar{A}\bar{B}\bar{C}P + \bar{A}\bar{B}CP + \bar{A}BC\bar{P} + \bar{ABC}\bar{P} + ABC\bar{P} + A\bar{B}\bar{C}P$$

$$11000 = \bar{A}\bar{B}(\bar{C}P + CP) + \bar{A}B(\bar{C}P + CP) +$$


$$11011 = \bar{A}B(C\bar{P} + CP) + A\bar{B}(\bar{C}P + CP)$$

$$11101 = \bar{A}\bar{B}(C\oplus P) + A\bar{B}(C\oplus P) + \bar{A}B(C\oplus P)$$

$$11110 = \bar{A}\bar{B}(C\oplus P) + A\bar{B}(C\oplus P) + \bar{A}B(C\oplus P)$$

$$= (C\oplus P)(\bar{A}\bar{B} + A\bar{B}) + (C\overline{\oplus P})(\bar{A}B + A\bar{B}) \\ = (C\oplus P)(A\overline{\oplus B}) + (\overline{C\oplus P})(A\oplus B)$$
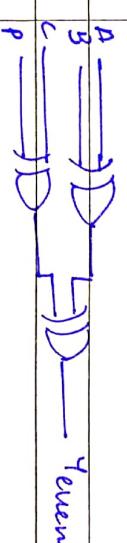
$$= C\oplus P \oplus A \oplus B \\ = A \oplus B \oplus C \oplus P$$



Design odd parity checker for 3 bit binary data
 & even no. of ones must be even to make it odd add one.

Parity

PL


00010
00100
00110
01000
01010
01100
01110
10000

		Kmap				
		AB	cp	00	01	10
0001	1	0	1	0	1	0
0100	0	0	1	0	1	0
0101	1	0	1	0	1	0
0110	1	1	0	1	0	1
0111	0	0	0	1	0	1

$$\begin{aligned}
 1001 &= \bar{A}\bar{B}\bar{C}\bar{P} + \bar{A}\bar{B}C\bar{P} + \bar{A}B\bar{C}\bar{P} + \bar{A}B\bar{C}P + A\bar{B}\bar{C}\bar{P} + A\bar{B}C\bar{P} \\
 1010 &= 1 \quad A\bar{B}\bar{C}\bar{P} + A\bar{B}C\bar{P} \\
 1011 &= \underline{\bar{A}\bar{B}} \quad (\bar{C}\bar{P} + C\bar{P}) + \bar{A}\bar{B} (C\bar{P} + C\bar{P}) + AB (\bar{C}\bar{P} + C\bar{P}) \\
 1100 &= 1 \quad + \bar{A}\bar{B} (\bar{C}\bar{P} + C\bar{P}) \\
 1101 &= 0 \quad = \bar{A} (\bar{C}\bar{P}) \quad (\bar{A}\bar{B} + AB) + C\bar{A}P (A\bar{B} + AB) \\
 1110 &= 0 \quad = \bar{A} (\bar{C}\bar{P}) \quad (\bar{A}\bar{B} + AB) + C\bar{A}P (A\bar{B} + AB) \\
 1111 &= 1 \quad = \bar{A} (\bar{C}\bar{P}) \quad (\bar{A}\bar{B} + AB) + C\bar{A}P (A\bar{B} + AB)
 \end{aligned}$$

Fus

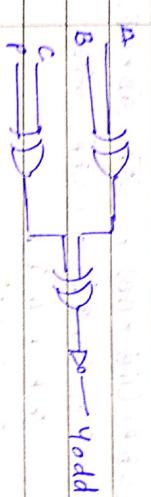0000
0001
0010
0011
0100
0101
0110
0111
1000
1001
1010
1011
1100
1101
1110
1111




— / —

Programmable logic Devices


PAL Programmable Array Logic
PLA Programmable logic Array

1) PAL

↓ ↓ Up

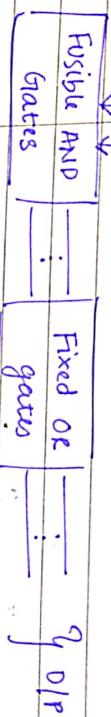

2) PLA

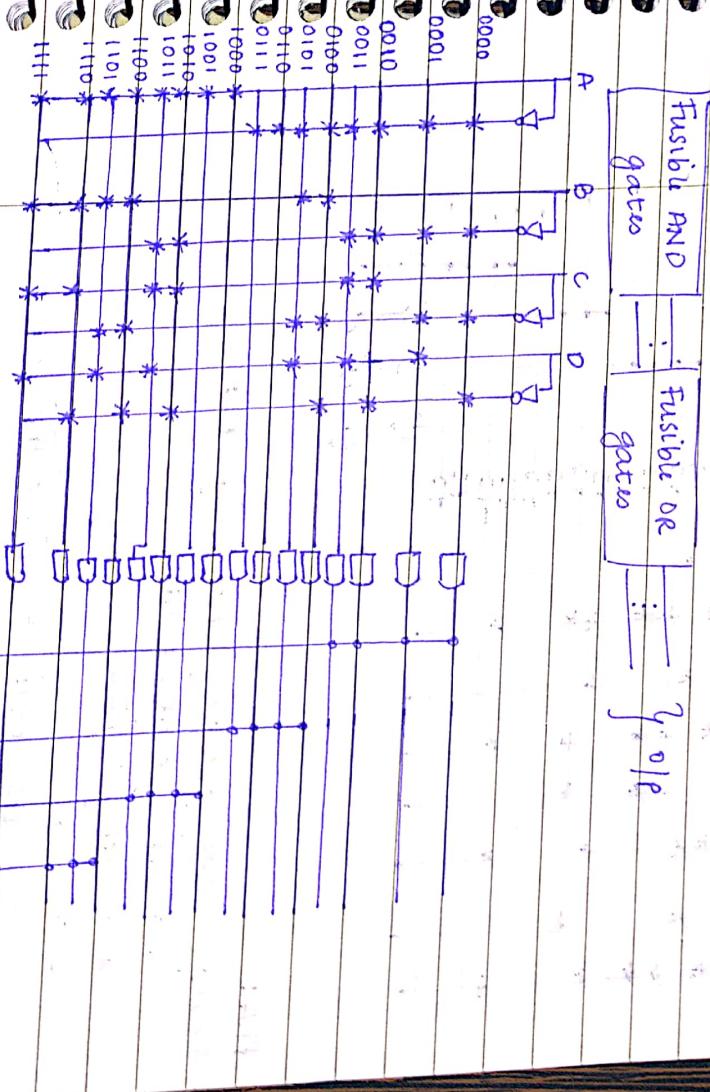

Generate the following BF using PLA


$$Y_3 = \bar{A}\bar{B}C\bar{D} + A\bar{B}C\bar{D} + \bar{A}B\bar{C}D + A\bar{B}CD$$

$$Y_2 = \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}D$$

$$Y_1 = AB\bar{C}D + \bar{A}\bar{B}CD$$

$$Y_0 = ABCD$$

4 AND gate for each B-functions

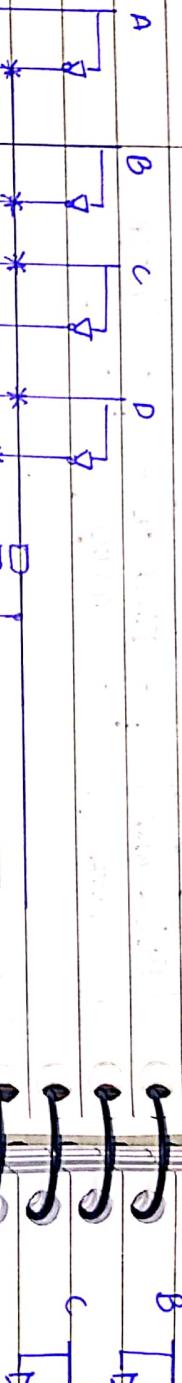

No. of m
[excluded]

No. of
m

m

m

m

m

m

m

m

m

m

m

m

m

m

m

m

m

m

m

m

m

m

m

m

m

m

PLA:

Realize the following BF using PLA

$$X = \bar{A}\bar{B}C + A\bar{B}C + ABC$$

$$Y = A\bar{B}\bar{C} + \bar{A}B\bar{C}$$


$$Z = \bar{B}C$$

$$= BC(A + \bar{A}) = A\bar{B}C + \bar{A}\bar{B}C$$

Realize
F1
F2

No. 6

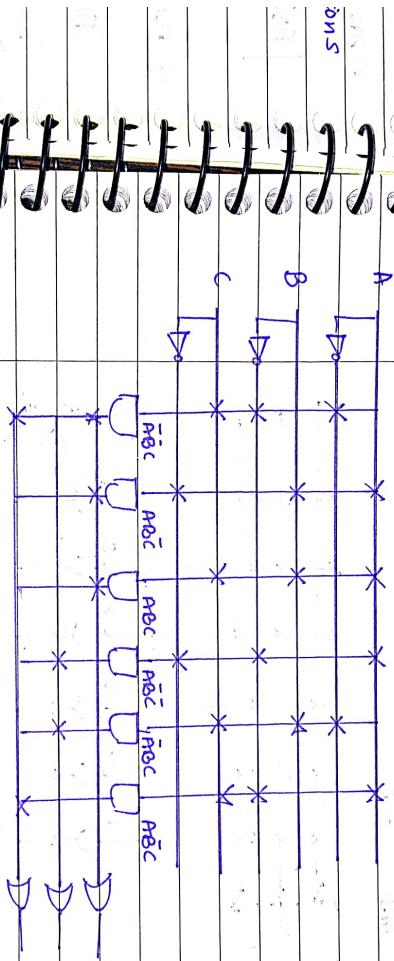No. of minterms = 6 = AND
 (excluding redundant minterms (repeated))
 No. of boolean functions = 3 = OR




Realize the following exp. using PEA

$$\rightarrow F_1(x_1, y_1, z) = \Sigma_m (3, 6, 7)$$

$$\rightarrow F_2(y_1, y_2, z) = \Sigma_m (0, 1, 2, 6, 7)$$

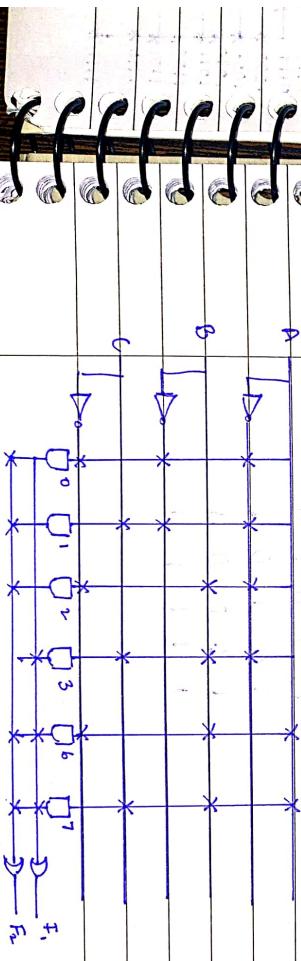No. of boolean functions = 2 = OR gates
 " minterms = 6 = AND gates



$c_{in} \rightarrow$ carry generated from prev addition
 $(out \rightarrow)$ " present addition

Realize using PLA


2) $F_1(n, y_1, 2) = E_m(1, 2, 3, 4)$

$$F_1(n, y_1, 2) = E_m(3, 5, 7)$$

$$\text{No. of gates} = 2$$

$$\text{AND} = 6$$

$$\begin{array}{c|cc|c} & 0 & 1 & \\ \Delta & \backslash & & \\ \Delta & 0 & 0 & 0 \\ & + & & \\ & 0 & 0 & 0 \\ \hline & 0 & 0 & 0 \end{array}$$

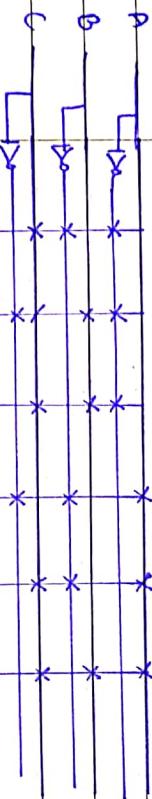

$$S = \bar{A}_1$$


$$+ A_1$$

$$= \bar{A}$$

$$= 1$$

$$S =$$

Real

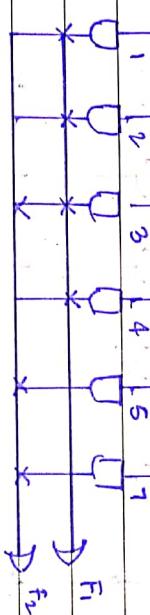

Full Adder [1 bit]

A' B' C' in S' Cout

A	B	Cin	1bit	S	0 0 0 0 0	0 0 1 1 0	0 1 0 1 0	1 0 1 0 1	1 0 0 1 0	1 0 0 1 0	1 0 0 1 0
0	0	0	0	0	0 0 0 0 0	0 0 1 1 0	0 1 0 1 0	1 0 1 0 1	1 0 0 1 0	1 0 0 1 0	1 0 0 1 0
1	0	0	1	1	1 1 1 1 1	1 1 0 0 1	0 1 1 1 0	0 1 0 1 1	1 0 1 0 1	1 0 0 1 1	1 0 0 1 1
1	1	1	1	1	1 1 1 1 1	1 1 0 0 1	0 1 1 1 0	0 1 0 1 1	1 0 1 0 1	1 0 0 1 1	1 0 0 1 1

K-map for S

K-map for Cout

A \ C _{in}	00	01	11	10	A \ C _{in}	00	01	11	10
0	0	(1)	0	(1)	0	0	0	(1)	0
1	(1)	0	(1)	0	1	0	(1)	1	(1)


$$\begin{aligned}
 S &= \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + \bar{A}\bar{B}\bar{C}_{in} \\
 &\quad + AB\bar{C}_{in} \\
 &= \bar{A}(\bar{B}C_{in} + BC_{in}) + A(\bar{B}\bar{C}_{in} + BC_{in}) \\
 &= \bar{A}(B \oplus C_{in}) + A(B \oplus \bar{C}_{in})
 \end{aligned}$$

$$S = A \oplus (B \oplus C_{in})$$

Realization

Sum

Cout

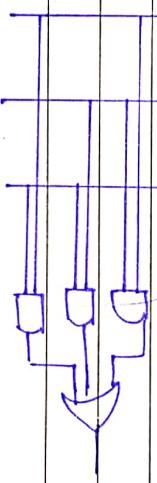

$$Cout = AC_{in} + BC_{in} + C_{in}A$$